

Indian Institute of Information & Technology,

Bhopal

ECE 6th Sem.

Minor Project -2023

Group No.

Group 10

Scholar No.	Student Name
20U01047	ABHISHEK BRAJVASI
20U01041	ARPEET BHAI SARE
20U01052	SRIRAMA ANIKETH
20U01024	SAMARTH VARSHNEY
Supervisor	
Dr. Bhupendra Singh Kirar	

Sign

Simple Clap Switch Circuit using CD4017

We are going to make Clap Operated Switch using CD4017 Decade counter IC. It consists of a condenser microphone that senses the clap sound and gives a clock pulse to the Decade counter IC which in response turns the ON or OFF the relay. This relay can switch AC loads or appliances. To increase the sensitivity of the circuit two transistors are added to the circuit.

WHAT IS A CD4017 IC?

It is a 16-pin IC having 11 pins as an output, 3 control pins which are reset, clock and active low enable, and two power pins that are V_{cc} and ground.

CD4017 APPLICATIONS

CD4017 has many applications which include Decoder, Binary counter, Frequency division, Decade counter, electronics projects like Remote controlled Switch, Light Chasers, Touch ON-OFF switches, Alarms, Clap switches, etc. This IC can be easily used where turning ON and OFF application is required.

CIRCUIT DIAGRAM

